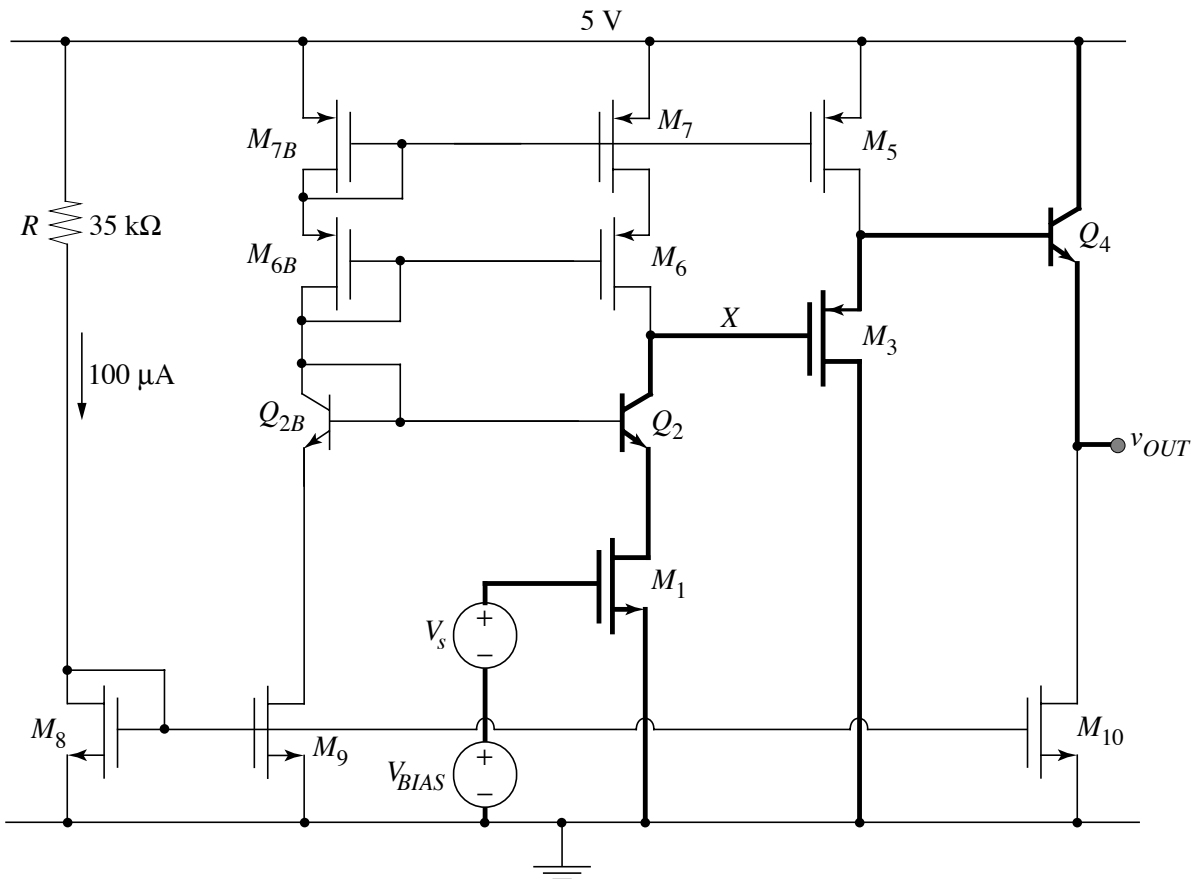


# Voltage Amplifier Frequency Response

## ■ Chapter 9 multistage voltage amplifier



## ■ Approaches:

1. brute force OCTC -- do for all capacitances in the circuit
2. identify the largest contributor(s) and calculate the Thévenin resistance associated with them

Try second approach: identify four nodes in signal path

## Qualitative Evaluation of Time Constants

- Input node: no contribution since  $R_S = 0$
- Drain of  $M_1$ : “low impedance node” since  $R_{in(CB)} = 1/g_{m2}$
- Node  $X$ : extremely high resistance ... could be a big time constant
- Source of  $M_3$ : “low impedance node” since  $R_{out(CD)} = 1/g_{m3}$
- Output node: “low impedance node” since  $R_{o(CC)} = 1/g_{m4}$

**Note:** we are *not* considering capacitances *between* nodes here ... since we are doing an approximate analysis, we will use Miller’s theorem to find their effective capacitance to ground

## Small-Signal Model of Node X

- Account for all of the capacitances from node X to *small-signal* ground:
  1. Base-collector capacitance  $C_{\mu 2}$  of  $Q_2$  (since it is connected to diode-connected transistors  $M_{6B}$  and  $M_{7B}$  that are in turn connected to  $V_{DD}$ )
  2. Gate-drain capacitance  $C_{gd6}$  of  $M_6$  (since it is connected to the same node as  $C_{\mu 2}$ )
  3. Gate-drain capacitance  $C_{gd3}$  of  $M_3$  (since it is connected directly to ground)


*Omitted* from Section 10.7's analysis: parasitic capacitances to substrate --  $C_{cs2}$  and  $C_{db6}$  are both present between node X and ground

  4. Effective capacitance due to  $C_{gs3}$  connected between the input and the output of the common-drain stage:

$$C_{eff} = C_{gs3}(1 - A_v C_{gs3})$$

The gain across  $C_{gs3}$  is about 1, but an accurate calculation would include any backgate effect on  $M_3$  if present.

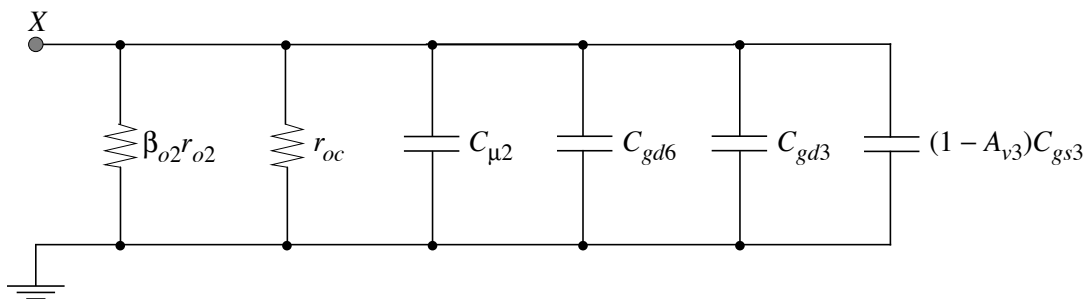- Small-signal model with all (non-parasitic) capacitances



## Gain-Bandwidth Product

- Considering only the time constant from node X

$$\omega_{3dB} \approx \frac{1}{[(\beta_{o2}r_{o2} || g_{m6}r_{o6}r_{o7})](C_{\mu 2} + C_{gd6} + C_{gd3} + (1 - A_v C_{gs3})C_{gs3})}$$

- Approximate low-frequency gain -- from Chapter 9


$$A_{vo} \approx -g_{m1}(\beta_{o2}r_{o2} || g_{m6}r_{o6}r_{o7})$$

- Gain-bandwidth product

$$|A_{vo}| \omega_{3dB} \approx \frac{g_{m1}}{C_{\mu 2} + C_{gd6} + C_{gd3} + (1 - A_v C_{gs3})C_{gs3}}$$

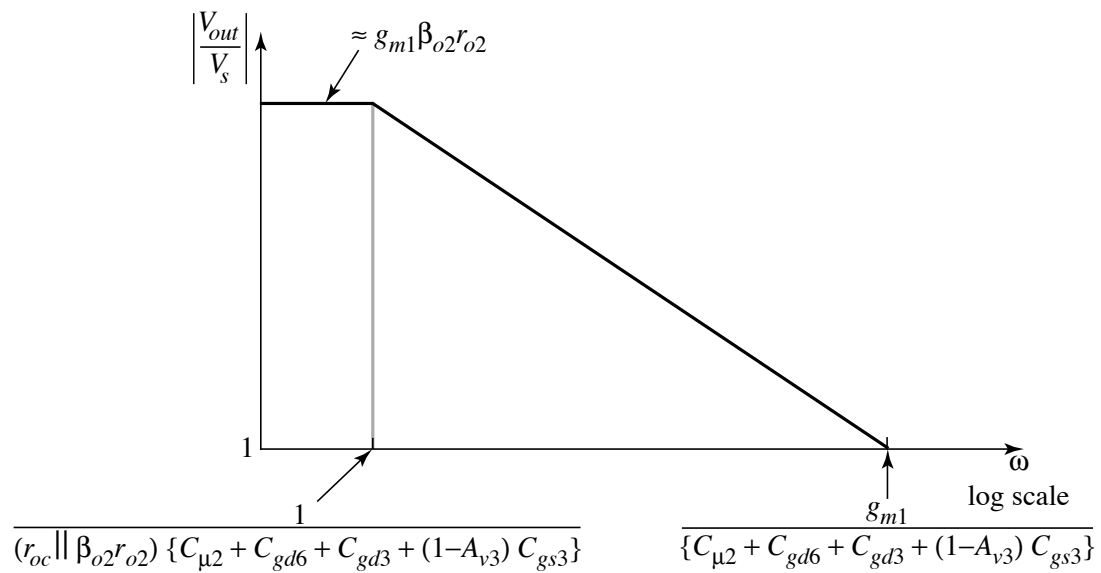
## Magnitude Bode Plot

- Assuming that the second pole is greater than the unity gain frequency, the Bode plot is


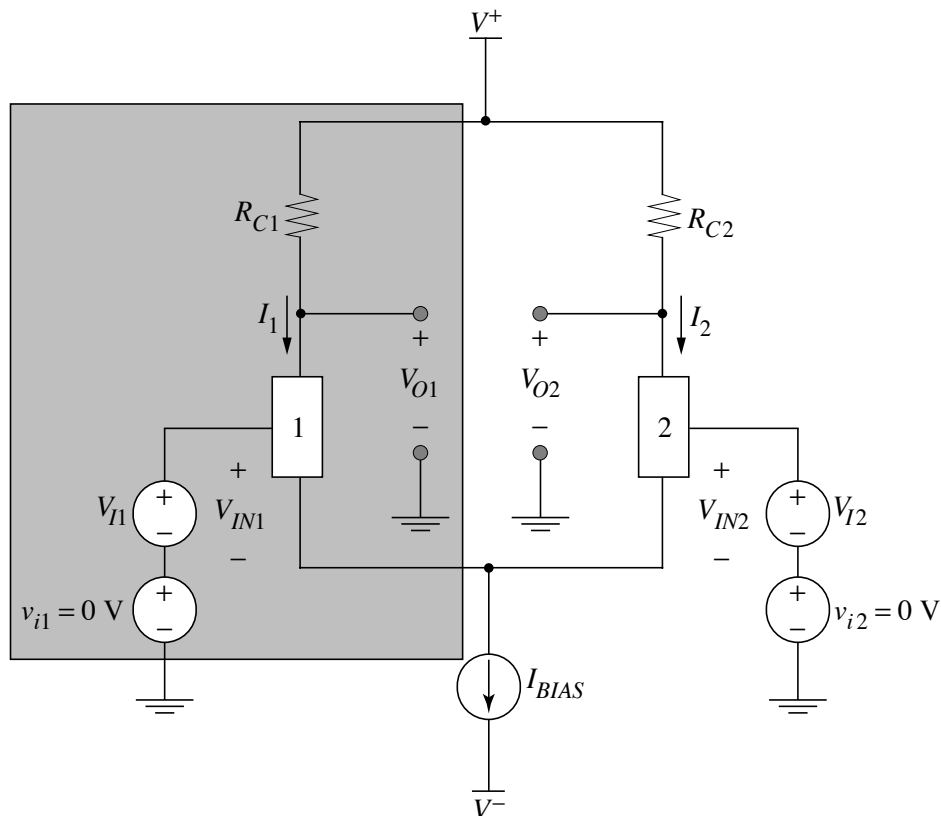
# Differential Amplifiers

- General structure: two inputs, two outputs



Consider balanced situation:  $V_{I1} = V_{I2}$  and  $R_{C1} = R_{C2}$  and devices 1 and 2 are in their constant-current modes.

$$I_{BIAS} = I_1 + I_2 = 2(V^+/R_C)$$

Adjust so  $V_{O1} = V_{O2}$  are about 0 V (note the dual supplies)

## Decomposition of Small-Signal Input Voltages

- Inputs  $v_{i1}$  and  $v_{i2}$  are *not* the “natural inputs” to understand how the differential amplifier works ...

- Define two new voltages


**differential-mode input voltage** =  $v_{id} = v_{i1} - v_{i2}$

**common-mode input voltage** =  $v_{ic} = (1/2)(v_{i1} + v_{i2})$

- Expressing the inputs  $v_{i1}$  and  $v_{i2}$  in terms of  $v_{id}$  and  $v_{ic}$


$$v_{i1} = v_{ic} + \frac{v_{id}}{2}$$

$$v_{i2} = v_{ic} - \frac{v_{id}}{2}$$

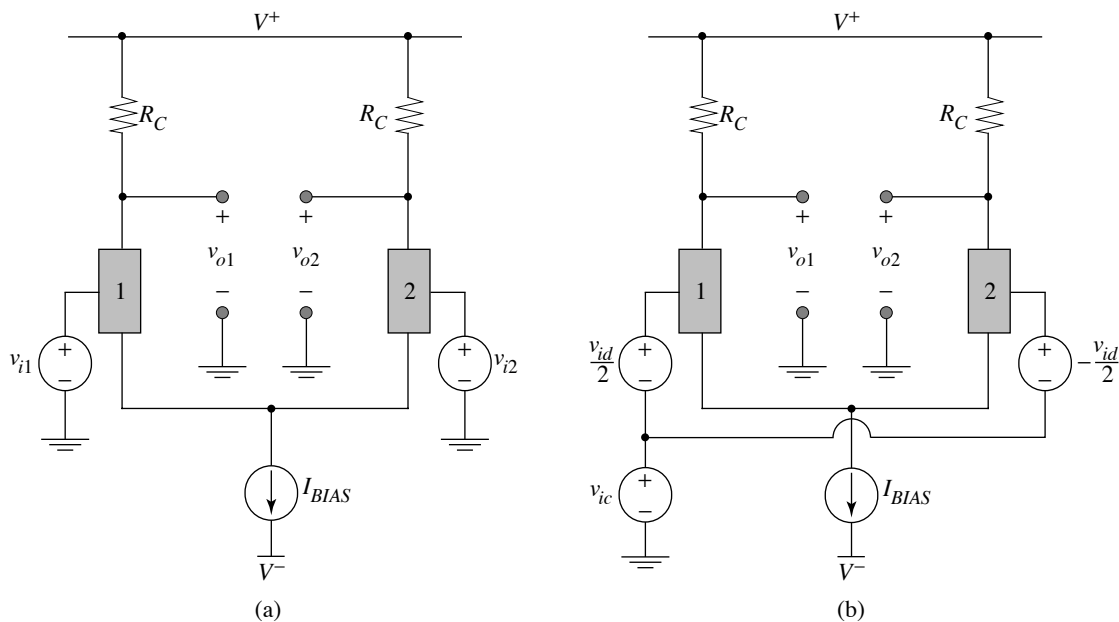
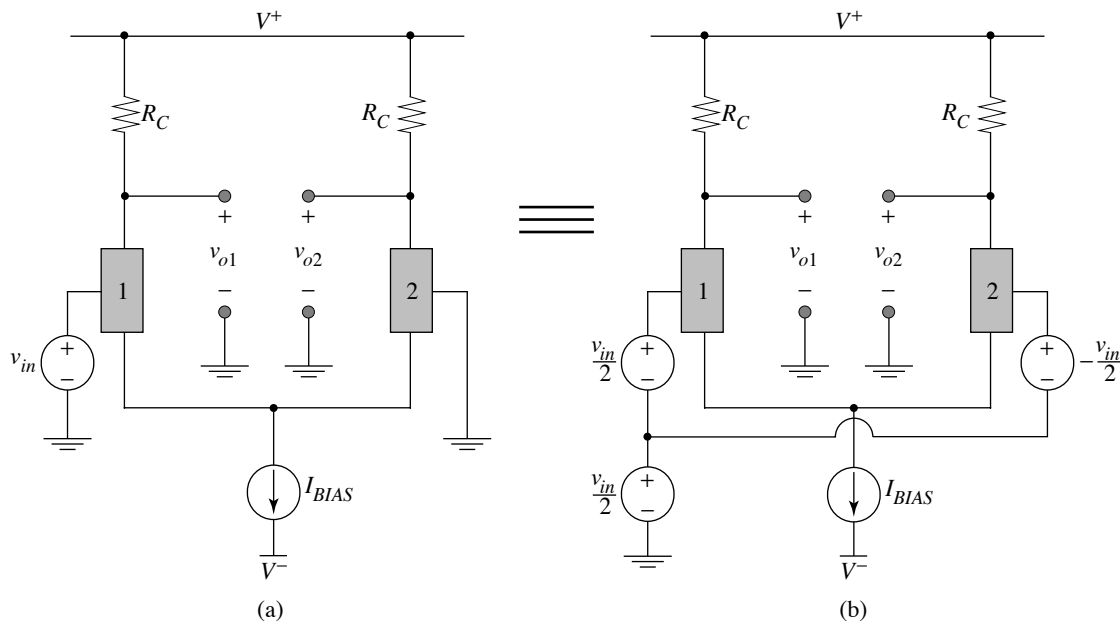
## Example of Signal Decomposition


- $v_{i1} = v_{in}$  and  $v_{i2} = 0$  V results in both a differential-mode and a common-mode input to the amplifier




- Goal:  
determine the response of the differential amplifier to  $v_{id}$  and  $v_{ic}$  separately and then reconstruct the response
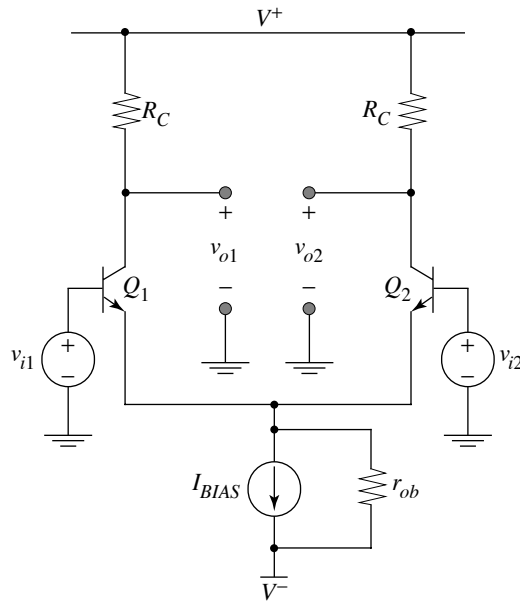
# Small-Signal Model of Bipolar Diff. Amplifier

- Define  $r_{ob}$  as the internal (source) resistance of the bias current source




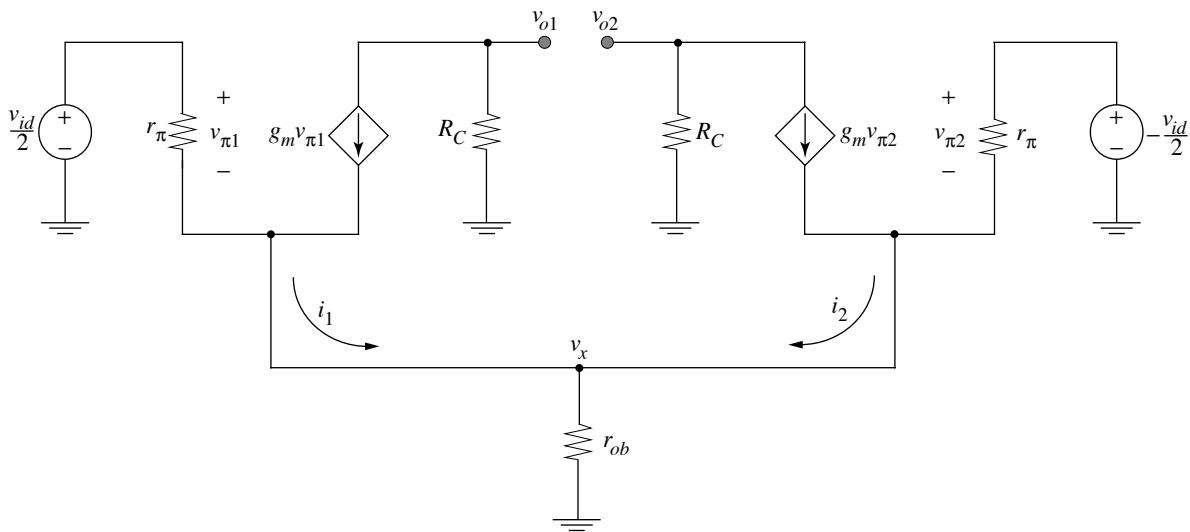- Small-signal model with **purely differential** inputs


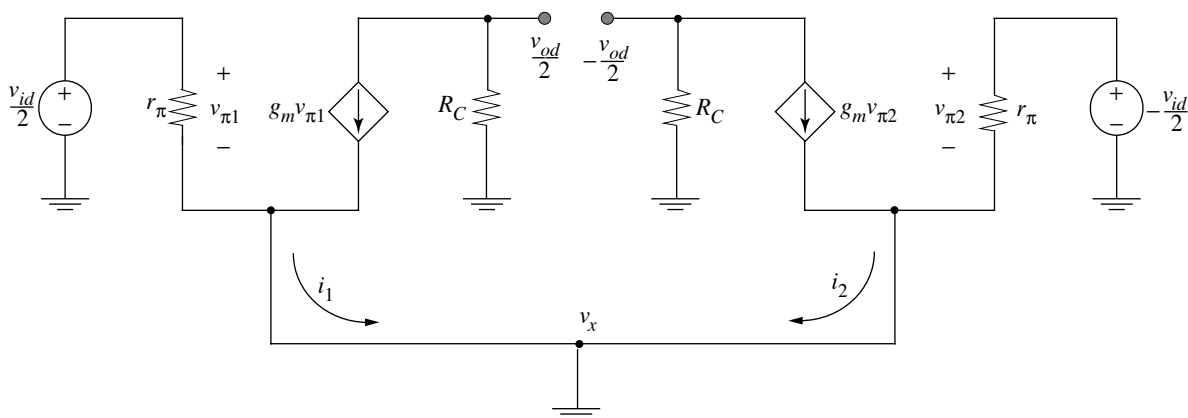
## Small-Signal Model with Purely Differential Inputs

- The voltage at  $v_x$  must be zero for purely differential inputs --> it can be considered a small-signal or incremental ground reference
- Only need to solve half of the circuit, whose outputs are + or -  $v_{od}/2$



- Solve left half to find

$$\frac{v_{od}}{2} = -g_m R_C \frac{v_{id}}{2}$$

define **differential-mode gain**  $a_{dm}$  by

$$a_{dm} = \frac{v_{od}}{v_{id}} = -g_m R_C$$